



ST. LAWRENCE HIGH SCHOOL

A Jesuit Christian Minority Institution



WORKSHEET -18 (ANSWER KEY)

Topic – JK, Master-Slave, D and T flip flops

Subject: COMPUTER SCIENCE

Class - 12

F.M:15

Chapter: Sequential Logic Circuits

Date: 22/06/2020

Choose the correct answer for each question:

[15 X 1 = 15]

1. In J-K flip-flop, if $J = 1$ and $K=0$ the output is said to be _____
 - a) **Set**
 - b) Reset
 - c) Previous state
 - d) Current state
2. In a J-K flip-flop, if $J=K$ the resulting flip-flop is referred to as _____
 - a) D flip-flop
 - b) S-R flip-flop
 - c) **T flip-flop**
 - d) S-K flip-flop
3. Both the J-K & the T flip-flop are derived from the basic _____
 - a) S-R flip-flop
 - b) **S-R latch**
 - c) D latch
 - d) D flip-flop
4. The flip-flops which has not any invalid states are _____
 - a) S-R, J-K, D
 - b) S-R, J-K, T
 - c) J-K, D, S-R
 - d) **J-K, D, T**
5. What does the triangle on the clock input of a J-K flip-flop mean?
 - a) Level enabled
 - b) **Edge triggered**
 - c) Both Level enabled & Edge triggered
 - d) Level triggered
6. What does the circle on the clock input of a J-K flip-flop mean?
 - a) Level enabled
 - b) Positive edge triggered
 - c) **negative edge triggered**
 - d) Level triggered

7. What does the direct line on the clock input of a J-K flip-flop mean?
- a) Level enabled
 - b) Positive edge triggered
 - c) negative edge triggered
 - d) **Level triggered**
8. In a positive edge triggered JK flip flop, a low J and low K produces?
- a) High state
 - b) Low state
 - c) Toggle state
 - d) **No Change State**
9. S-R type flip-flop can be converted into D type flip-flop if S is connected to R through _____
- a) OR Gate
 - b) AND Gate
 - c) **Inverter**
 - d) Full Adder
10. When both the inputs J and K have a HIGH state, the flip-flop switches to
- a) set
 - b) reset
 - c) **complement state**
 - d) undefined
11. In J-K flip-flop, if $J = 0$ and $K = 1$ the output is said to be _____
- a) Set
 - b) **Reset**
 - c) Previous state
 - d) Current state
12. The following flip-flop is used as latch:
- a) JK flip flop
 - b) **D flip-flop**
 - c) T flip-flop
 - d) SR flip-flop
13. What kind of drawback of SR flip-flop is removed by JK flip-flop?
- a) $S=0, R=0$
 - b) $S=0, R=1$
 - c) $S=1, R=0$
 - d) **$S=1, R=1$**
14. The output Q can be clocked low by setting JK input to:
- a) 1,1
 - b) 1,0
 - c) **0,1**
 - d) 0,0

15. JK flip flop has
- a) temporary memory
 - b) no memory
 - c) **true memory**
 - d) random memory

Phalguni Pramanik