



STUDY MATERIAL - 3 (PART - II)

Subject : PHYSICS

CLASS : XII

Date : 8.6.20

Chapter : Electrostatics

Topic : Capacitor


D : Short Notes

1. **Capacitors** : A capacitor is a device to store charge or electrostatic energy.

Capacitance : It is the capacity of the capacitor to store charge. In a capacitor $Q \propto V$ or $Q = CV$; C is called the capacitance.

$$C = (M^{-1}L^{-2}T^4A^2)$$

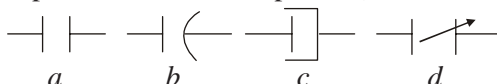The following Fig. (a) or (b) represent circuit symbol for a simple capacitor. The Fig. (c) represents electrolytic and Fig (d) represents variable capacitor (tuner or trimmer).



From the point of view of the shape of capacitors, they are of three types : spherical, parallel plate and cylindrical.

Unit of capacitance is Farad $1F = \frac{1C}{1V}$.


1F is a very big unit. Therefore smaller units like μF , nF or $\mu\mu F$ (also called pF) are used very commonly.

Spherical Capacitors : These are of two types :

- (a) **Isolated spherical capacitors** (b) **Concentric spherical capacitors**

- (a) Isolated spherical capacitor consists of a single sphere. Its capacitance $C = 4\pi\epsilon_0 R$ i.e. $C \propto R$ where R is radius of the sphere. See the Fig.

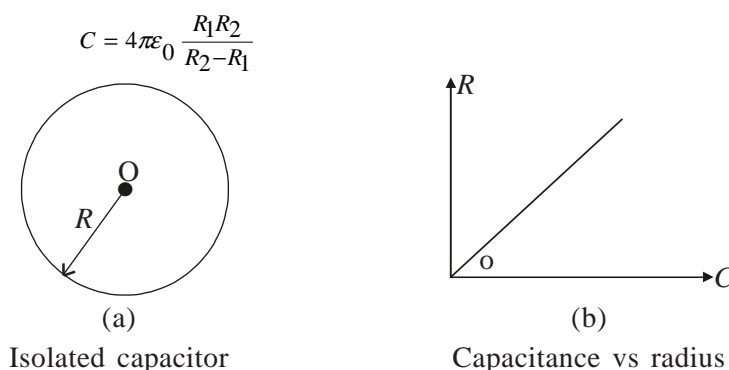- (b) Two spherical shells (or inner one may be solid) form a concentric spherical capacitor as shown in the following figure. Note that normally outer sphere is grounded.



If a dielectric of strength K is introduced between R_1 and R_2

$$C = 4\pi\epsilon_0 K \frac{R_1 R_2}{R_2 - R_1}$$

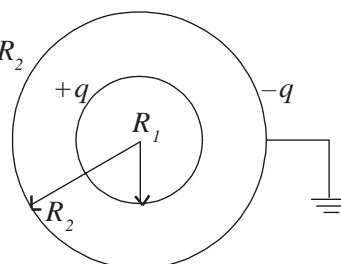


Fig. Concentric shell capacitor

2. Parallel Plate Capacitor :

If two plates each of area A are separated by a distance d in vacuum as shown in the Figure.

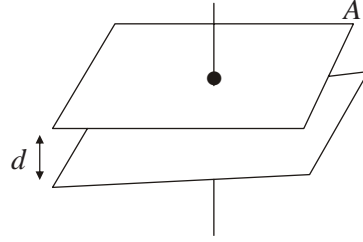


Fig. Parallel plate capacitor

then $C = \frac{\epsilon_0 A}{d}$

$C = \frac{k\epsilon_0 A}{d}$ if a dielectric of strength k is completely filled in the gap.

$C = \frac{\epsilon_0 A}{d-t\left(1-\frac{1}{k}\right)}$ if the dielectric slab has thickness $t(t < d)$

3. Force between the plates of a capacitor is attractive and its magnitude is $F = \frac{Q^2}{2A\epsilon_0}$

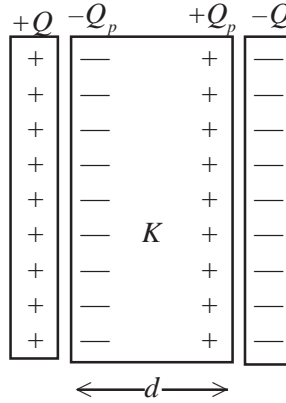


Fig. Polarization illustration

4. Energy stored in a capacitor

$$U = \frac{1}{2} CV^2 = \frac{QV}{2} = \frac{Q^2}{2C}$$

If the charge is uniformly distributed throughout the volume then energy stored $U = \frac{1}{2} \int V_p dv$ where dv is volume element and V is potential difference. Volume density of electric field energy

$$u = \frac{E\sigma}{2} = \frac{\epsilon_0 E^2}{2} \text{ in free space}$$

volume density of electric field energy in a medium $u_{med} = \frac{\epsilon_0 k E^2}{2} = \frac{\epsilon_0 \epsilon_r E^2}{2}$.

5. **Capacitor in series :** In series magnitude of the charge on each plate is equal but voltage across each capacitor is different.

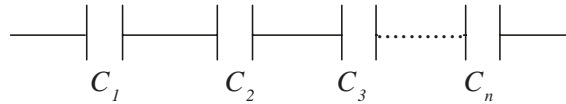


Fig. Capacitors in series

$$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_n}$$

If n equal capacitors are in series then $C_{eq} = \frac{C}{n}$

6. **Capacitors in Parallel**

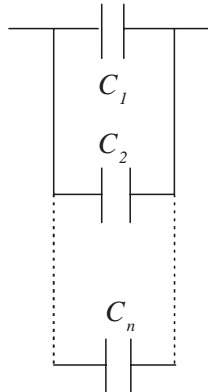


Fig : Capacitors in Parallel

If $C_1, C_2, C_3, \dots, C_n$ are connected in parallel as shown in the above figure then

$$C_{eq} = C_1 + C_2 + C_3 + \dots + C_n$$

Note that in parallel, charge on each capacitor is different while potential drop or voltage across each capacitor is equal. If n equal capacitors are in parallel then $C_{eq} = nC$.


There are four methods to simplify capacitance networks

- Series parallel method
 - Wheatstone bridge method
 - Charge distribution method
 - Star/delta method.
7. **Charge Distribution Method :** It can be applied in principle anywhere in tune with Kirchhoff's law but in symmetrical circuits it makes the problem very simple. In symmetrical circuits charge entering a branch — charge leaving the branch (identical) or mirror image branch.

If two capacitors C_1 and C_2 charged to V_1 and V_2 are joined together then common potential is

$$V_{common} = \frac{V_1 C_1 + V_2 C_2}{C_1 + C_2} = \frac{Q_1 + Q_2}{C_1 + C_2}$$

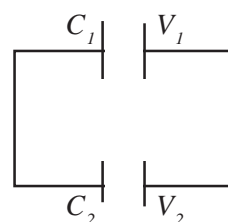Charge on capacitors after joining $\frac{Q_1'}{Q_2'} = \frac{C_1}{C_2}$



Common potential

Loss in energy when two capacitors C_1 and C_2 charged to V_1 and V_2 are joined together as shown in the figure is

$$\Delta E = \frac{C_1 C_2}{(C_1 + C_2)} (V_1 - V_2)$$


If dielectrics are added in the manner shown in the following fig. (a) then net capacitance is in a parallel combination of C_1 , C_2 and C_3 as illustrated in the fig. (b)

$$C_1 = \frac{\epsilon_0 k_1 A/3}{d},$$


$$C_2 = \frac{\epsilon_0 k_2 A/3}{d}$$

$$C_3 = \frac{\epsilon_0 k_3 A/3}{d} \text{ and}$$

$$C = C_1 + C_2 + C_3$$

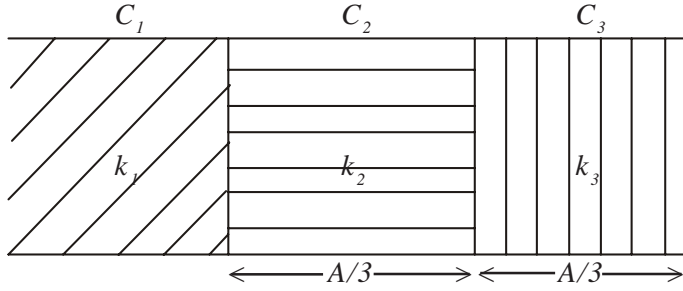

(a)

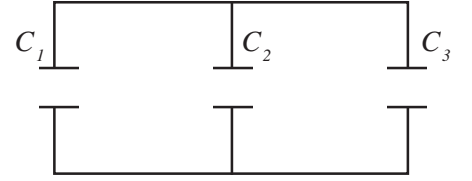

(b)

Fig. Effect of dielectrics on capacitor


If dielectrics are arranged as shown in Fig. (a) then C_{eq} IS series combination of C_1 , C_2 and C_3 as illustrated in Fig. (b).

$$C_1 = \frac{\epsilon_0 K_1 A}{\frac{d}{3}}$$


$$C_2 = \frac{\epsilon_0 K_2 A}{\frac{d}{3}}$$

$$C_3 = \frac{\epsilon_0 K_3 A}{\frac{d}{3}}$$
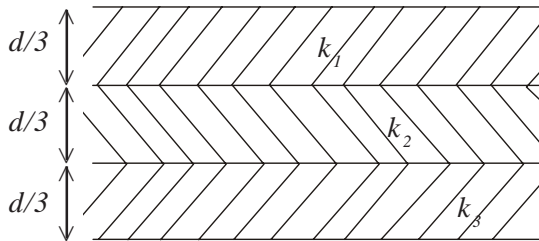
$$C_{eq} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} = \frac{d}{3\epsilon_0 A} \left[\frac{1}{k_1} + \frac{1}{k_2} + \frac{1}{k_3} \right]$$



(a)

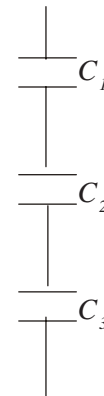

(b)

Fig. Effect of dielectrics in a capacitor

E. Exercise Problems :

1. A parallel plate capacitor with plate area 100 cm^2 and separation between the plate 5 mm is connected across a 24 V battery. The force of attraction between the plates is of the order of —

$$\begin{aligned} \text{Ans. : } F &= \frac{Q^2}{2A\epsilon_0} = \frac{(CV)^2}{2A\epsilon_0} = \frac{\left(\frac{A\epsilon_0}{d}\right)^2 V^2}{2A\epsilon_0} \\ &= \frac{A\epsilon_0 V^2}{2d^2} = \frac{10^{-2} \times 8.85 \times 10^{-12} \times 24^2}{2 \times 25 \times 10^{-6}} = 1.08 \times 10^{-6} \text{ N.} \end{aligned}$$

2. A capacitor $10 \mu\text{F}$ charged to 50 V is joined to another uncharged $50 \mu\text{C}$ capacitor. Find the loss in energy.

$$\text{Ans : Energy loss} = \frac{C_1 C_2}{2(C_1 + C_2)} (V_1 - V_2)^2 = \frac{10 \times 50 \times 10^{-12}}{2(10 + 50) \times 10^{-6}} (50 - 0)^2 = 1.04 \times 10^{-4} \text{ J}$$


3. Two spheres of radius 5 cm and 10 cm , both charged to $120 \mu\text{C}$, are joined by a metal wire and then metal wire is removed. What is the charge on each after removal of the wire?

$$\begin{aligned} \text{Ans : } Q_1' &= \frac{(Q_1 + Q_2)r_1}{r_1 + r_2} = \frac{240 \times 5}{15} = 80 \mu\text{C} \\ Q_2' &= 240 - 80 = 160 \mu\text{C} \end{aligned}$$

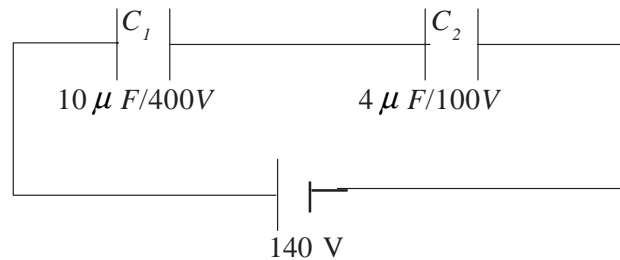4. A $10 \mu\text{F}/400 \text{ V}$ and a $4 \mu\text{F}/100 \text{ V}$ capacitors are connected in series. Find the maximum potential which can be applied.

Ans : The maximum charge which can be applied is $400 \mu\text{C}$ (maximum rating of $4 \mu\text{F}/100 \text{ V}$ capacitor).

Thus, potential which can be applied is $100 + 40 = 140 \text{ V}$.




5. In the circuit shown, a potential difference of 60 V is applied across AB . The potential difference between the points M and N is

Ans : Let Q amount of charge flow through the MN branch

$$V = 60 \text{ V} = \frac{Q}{2C} + \frac{Q}{C} + \frac{Q}{2C} = 2 \frac{Q}{C} \quad \text{or } Q = 30C \text{ V.}$$
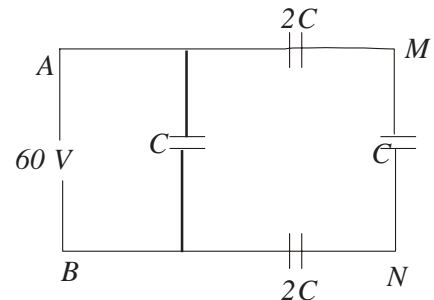
$$\begin{aligned} \text{Potential difference between } M \text{ and } N &= \frac{Q}{C} = \frac{30C}{C} \text{ V} \\ &= 30 \text{ V} \end{aligned}$$



Ambarnath Banerjee