



WORKSHEET – 2

TOPIC – LOGIC GATES & COMBINATIONAL CIRCUITS

SUBJECT: COMPUTER APPLICATION
F.M.: 15

CLASS: XII
DATE: 04.05.2020

➤ Choose the correct option:

(1X15=15)

1) Which of the following gates is called a universal gate? :

- (a) NOT (b) XNOR (c) NAND (d) XOR

2) All types of logic gates can be formed by suitable combinations of _____ gates only:

- (a) NOT (b) AND (c) NOR (d) XOR

3) How many NAND gate(s) are required to form an AND gate? :

- (a) 1 (b) 2 (c) 3 (d) 4

4) How many NAND gate(s) are required to form an OR gate? :

- (a) 1 (b) 2 (c) 3 (d) 4

5) The output of a 2 input XOR gate with inputs A and B is given by:

- (a) AB (b) $\overline{A}B + A\overline{B}$ (c) $\overline{A} \overline{B} + AB$ (d) A+B

6) The output of a 2 input XNOR gate with inputs A and B is given by:

- (a) AB (b) $\overline{A}B + A\overline{B}$ (c) $\overline{A} \overline{B} + AB$ (d) A+B

7) How many NOR gate(s) are required to form an AND gate? :

- (a) 3 (b) 2 (c) 1 (d) None of these

8) How many NOR gate(s) are required to form an OR gate? :

- (a) 3 (b) 2 (c) 1 (d) None of these

9) How many NOR gate(s) are required to form a NOT gate? :

- (a) 4 (b) 3 (c) 2 (d) 1


10) How many NAND gate(s) are required to form a NOT gate? :

- (a) 4 (b) 3 (c) 2 (d) 1

11) NAND gate is called an:


- (a) Uniform Gate (b) Universal Gate (c) Unilateral Gate (d) Unidigital Gate

12) The following symbol is of:

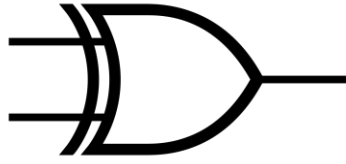

- (a) NOT (b) XOR (c) NAND (d) XNOR

13) The following symbol is of:

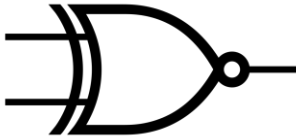

- (a) NOT (b) XOR (c) NAND (d) XNOR

14) $\overline{A}B + A\overline{B}$ may also be represented as:

- (a) $A \oplus B$ (b) $\overline{A \oplus B}$ (c) $A \cdot B$ (d) $A + B$

15) $\overline{A} \overline{B} + AB$ may also be represented as:

- (a) $A \oplus B$ (b) $\overline{A \oplus B}$ (c) $A \cdot B$ (d) $A + B$

PRITHWISH DE