



WORKSHEET – 7

TOPIC – LOGIC GATES & COMBINATIONAL CIRCUITS

SUBJECT: COMPUTER APPLICATION
F.M.: 15

CLASS: XII
DATE: 09.05.2020

➤ Choose the correct option:

(1X15=15)

1) A multiplexer circuit has:

- (a) one input, many outputs (b) many inputs, one output
(c) one input, one output (d) many inputs, many outputs

2) In a multiplexer, m control bits can be used to select a maximum of how many input lines?:

- (a) 2^m (b) m (c) 2m (d) m^2

3) For a 4X1 MUX, what is the number of inputs?:

- (a) 1 (b) 2 (c) 3 (d) 4

4) For a 8X1 MUX, what is the number of outputs?:

- (a) 1 (b) 2 (c) 3 (d) 4

5) Multiplexer is a/an _____ circuit:

- (a) Sequential (b) Odd (c) Even (d) Combinational

6) The number of OR gate(s) used for circuit diagram of 8X1 MUX will be:

- (a) 1 (b) 2 (c) 3 (d) 4

7) The number of AND gate(s) used for circuit diagram of 8X1 MUX will be:

- (a) 4 (b) 6 (c) 8 (d) 10

8) An AND-OR SOP circuit can be made using a:

- (a) Multiplexer (b) De - Multiplexer (c) Encoder (d) Decoder

9) For 3 control signals, what will be the number of outputs of a Multiplexer?:

- (a) 8 (b) 5 (c) 4 (d) 1

10) For 3 control signals, what will be the number of inputs of a Multiplexer?:

- (a) 8 (b) 5 (c) 4 (d) 1

11) If there are 16 inputs in a Multiplexer, what will be the number of control signals?:

- (a) 2 (b) 3 (c) 4 (d) 5

12) In a 4X1 MUX, 10 as control signal combination will give the output:

- (a) I_0 (B) I_1 (c) I_2 (d) I_3

13) Multiplexer means:

- (a) one to many (b) many to many (c) many to one (d) one to one

14) 3 bit control signals can be used to select _____ number of inputs:

- (a) 2 (b) 4 (c) 6 (d) 8

15) If the number of input is 10, the number of control signals required is:

- (a) 2 (b) 4 (c) 6 (d) 8

PRITHWISH DE