



ST. LAWRENCE HIGH SCHOOL

A Jesuit Christian Minority Institution



WORKSHEET -23

Topic – Ripple & Decade Counter

Subject: COMPUTER SCIENCE

Class - 12

F.M:15

Chapter: Sequential Logic Circuits

Date: 27/06/2020

Choose the correct answer for each question:

[15 X 1 = 15]

1. A down counter using n-flip-flops count _____
 - a) Downward from a maximum count
 - b) Upward from a minimum count
 - c) Downward from a minimum to maximum count
 - d) Toggles between Up and Down count
2. Which of the following statements are true?
 - a) Asynchronous events does not occur at the same time
 - b) Asynchronous events are controlled by a clock
 - c) Synchronous events does not need a clock to control them
 - d) Only asynchronous events need a control clock
3. UP Counter is _____
 - a) It counts in upward manner
 - b) It count in down ward manner
 - c) It counts in both the direction
 - d) Toggles between Up and Down count
4. DOWN counter is _____
 - a) It counts in upward manner
 - b) It count in downward manner
 - c) It counts in both the direction
 - d) Toggles between Up and Down count
5. How many different states does a 3-bit asynchronous down counter have?
 - a) 2
 - b) 4
 - c) 6
 - d) 8
6. In a 3-bit asynchronous down counter, the initial content is _____
 - a) 000
 - b) 111
 - c) 010
 - d) 101
7. A ripple counter's speed is limited by the propagation delay of _____
 - a) Each flip-flop
 - b) All flip-flops and gates
 - c) The flip-flops only with gates
 - d) Only circuit gates

8. A principle regarding most display decoders is that when the correct input is present, the related output will switch _____
- a) HIGH
 - b) To high impedance
 - c) To an open
 - d) LOW
9. Three decade counter would have _____
- a) 2 BCD counters
 - b) 3 BCD counters
 - c) 4 BCD counters
 - d) 5 BCD counters
10. BCD counter is also known as _____
- a) Parallel counter
 - b) Decade counter
 - c) Synchronous counter
 - d) VLSI counter
11. How many flip-flops are required to construct a decade counter?
- a) 4
 - b) 8
 - c) 5
 - d) 10
12. What happens to the parallel output word in an asynchronous binary down counter whenever a clock pulse occurs?
- a) The output increases by 1
 - b) The output decreases by 1
 - c) The output word increases by 2
 - d) The output word decreases by 2
13. The output of UP counters goes on increasing due to _____.
- a) Transmission of clock pulses
 - b) Reception of clock pulses
 - c) Both a and b
 - d) None of the above
14. How many flip-flops are required to construct a MOD-32 binary counter?
- a) 4
 - b) 8
 - c) 5
 - d) 10
15. If the output of two-bit asynchronous binary up counter using T flip flops is '00' at reset condition, then what output will be generated after the fourth negative clock edge?
- a) 00
 - b) 01
 - c) 10
 - d) 11