



St. Lawrence High School
A Jesuit Christian Minority Institution



Term : Pre – Test

Solution of Work Sheet – 18

Subject – Physical Science

Class – X

Date – 17.06.20

Chapter – Current Electricity

Topic – Electric cell

Choose the correct option for the following questions.

1 × 15 = 15

- For an ideal electric cell –
 - The emf is greater than its terminal voltage
 - The emf is equal to its terminal voltage
 - The internal resistance is zero
 - Both b. and c. are correct

Ans: d. Both b. and c. are correct
- Emf of an electrical cell is the –
 - Potential appear across the external load
 - Potential drop across its internal resistance
 - Difference of potential at its two ends when it is open circuited
 - None of these

Ans: c. Difference of potential at its two ends when it is open circuited
- For real electric cell –
 - Emf = Terminal voltage
 - Emf > Terminal voltage
 - Emf < Terminal voltage
 - Terminal voltage is = lost volt

Ans: b. Emf > Terminal voltage
- Lost volt is –
 - Potential appear across the external load
 - Potential drop across its internal resistance
 - Difference of potential at two ends of cell
 - None of these

Ans: b. Potential drop across its internal resistance
- Choose the correct option of a real electric cell.
 - Emf = terminal voltage – lost volt
 - Emf = lost volt – terminal voltage
 - Terminal voltage = emf +lost volt
 - Terminal voltage = emf – lost vilt

Ans: d. Terminal voltage = emf – lost vilt
- A battery of emf 15 volts and internal resistance 0.5 ohm is connected to an 11.5 ohm external resistance. The current through the external resistance will be –
 - 1.261 ampere
 - 7 ampere
 - 1.52 ampere
 - 1.25 ampere

Ans: d. 1.25 ampere

7. For the above circuit the terminal voltage is –

- a. 15 volts
- b. 14.375 volts
- c. 14.625 volts
- d. None of these

Ans: b. 14.375 volts

8. A 20 volt dc battery is connected to an external resistor of resistance 38 ohm. If the internal resistance of the battery is 2 ohm, then the lost volt is –

- a. 2.0 volt
- b. 1.5 volt
- c. 1.0 volt
- d. 0.5 volt

Ans: c. 1.0 volt

9. An electric bulb is connected to a 12 volt dc battery of internal resistance 1 ohm. If the resistance of the bulb is 23 ohm, then what is the power dissipated through the bulb?

- a. 4.25 watt
- b. 6 watt
- c. 12 watt
- d. 5.75 watt

Ans: d. 5.75 watt

10. In the above problem what is the power dissipated by the internal resistance of the battery?

- a. 12 watt
- b. 2.3 watt
- c. 0.25 watt
- d. 0 watt

Ans: c. 0.25 watt

11. Keeping the resistance unchanged, if the current through a conductor is doubled and the time duration is halved, then the amount of heat generated will be –

- a. Doubled
- b. Four times
- c. Half
- d. Four times

Ans: a. Doubled

12. The SI unit of electric power and the correct relation relating it is –

- a. Watt, Watt = Coulomb x time
- b. Watt, Watt = Coulomb x Volt
- c. Watt, Watt = Ampere x Volt
- d. Joule, Joule = Coulomb x Volt

Ans: c. Watt, Watt = Ampere x Volt

13. A 4.2 ohm resistance is connected to a battery for 30 min. If the current through the resistance is 1 A, then the energy dissipated by the resistance is –

- a. 1800 Joule
- b. 7560 joule
- c. 7650 Joule
- d. 8756 Joule

Ans: b. 7560 Joule

14. In the above problem the total heat produced by the resistance is –

- a. 7560 cal
- b. 6570 cal
- c. 5000 cal
- d. 1800 cal

Ans: d. 1800 cal

15. The power appear across a 10 ohm resistance is 160 watt. The current through the resistance is –

- a. 16 A
- b. 6 A
- c. 4 A
- d. 1.6 A

Ans: c. 4 A

Name of the teacher – Soumitra Maity