



ST. LAWRENCE HIGH SCHOOL
A JESUIT CHRISTIAN MINORITY INSTITUTION



STUDY MATERIAL - 4 (PART - II)

Subject : PHYSICS

Topic : Current Electricity

CLASS : XII

Date : 18.6.20

D : Numericals

- Exmple : A wire of length 6 m and area of cross-section 1 mm^2 carries a current of 2 A. If unit cubic meter of the material of a wire contains 10^{29} free electrons, find the average time taken by an electron to cross the length of the wire.


$$\text{Solution : } v = \frac{1}{neA} = \frac{2}{10^{29} \times 1.6 \times 10^{-19} \times 1 \times 10^{-6}} = 1.25 \times 10^{-4} \text{ ms}^{-1}$$

$$t = \frac{1}{v} = \frac{6}{1.25 \times 10^{-4}} = 4.8 \times 10^4 \text{ s} = 13.33 \text{ hr}$$

- The resistivity of a metallic wire is $1 \times 10^{-8} \Omega \text{ m}$. If the length of the metallic wire is doubled and its area of cross-section is made half, what will be the new value of the resistivity of the wire?

Solution : Since resistivity does not depend upon the physical dimensions i.e, length and area of cross-section of the material, so new resistivity will be unchanged i.e it remains $1 \times 10^{-8} \Omega \text{ m}$.

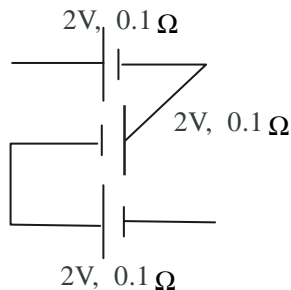- Find the total e.m.f. and total internal resistance of the group of cells shown below :




Solution : The cells are connected in series. Here, $n = 3$, $E = 2\text{V}$, $r = 0.1 \Omega$

$$E_{eq} = nE = 3 \times 2 = 6\text{V}$$

$$r_{eq} = nr = 3 \times 0.1 = 0.3 \Omega$$

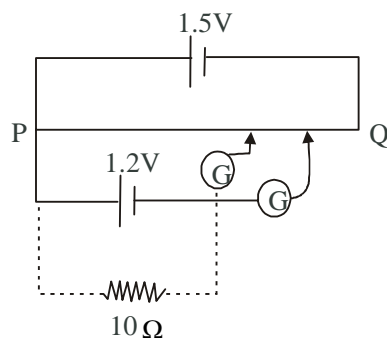- A potentiometer with 1.5 V cell is used for finding the internal resistance of a 1.2 V cell. The balance point comes at 65 cm. If a resistor of 10Ω is used as shown in the figure, the balance point changes to 55 cm. Calculate the internal resistance of the cell.



Solution : Here, $R = 10\Omega$, $l_1 = 65\text{ cm}$ and $l_2 = 55\text{cm}$

Internal resistance of the cell is given by,

$$r = \left(\frac{l_1 - l_2}{l_2} \right) R = \left(\frac{65 - 55}{55} \right) \times 10 = 1.82\Omega$$

5. What is the expression for determining unknown resistance by a meter bridge? [2012]

Soln. In case of a meter bridge, the unknown resistance

$$S = R \cdot \frac{Q}{P} = R \cdot \frac{100 - l}{l}$$

6. When a resistance of 7Ω is connected across the terminals of a cell, the current through the circuit is 1.1A. When the resistance is increased to 13Ω , the current is 0.67A. Determine the emf of the cell and its internal resistance. [2012]

Soln : Let the emf and internal resistance of the cell are E and r respectively.

In first case, current through the circuit,

$$l_1 = \frac{E}{R + r} \quad \text{or, } 1.1 = \frac{E}{7 + r} \quad \dots(1)$$

In second case, current through the circuit

$$l_2 = \frac{E}{R + r} \quad \text{or, } 0.67 = \frac{E}{13 + r} \quad \dots(2)$$

Solving (1) and (2) we get,

$$E = 10.28\text{ V and } r = 2.35\Omega$$

Ambarnath Banerjee