



ST. LAWRENCE HIGH SCHOOL
A JESUIT CHRISTIAN MINORITY INSTITUTION



WORK SHEET 23

Subject : PHYSICS

CLASS : XII

25.6.20

Chapter : Electromagnetism


Topic : Moving coil galvanometer, galvanometer as voltmeter and ammeter.

Multiple Choice Question :


1 x 15 = 15

1. For 1 A current, a galvanometer shows its full-scale deflection. If a resistance of $800\ \Omega$ is connected in series, it is converted into a voltmeter of range 0 - 1000 V. What is the resistance of the galvanometer ?
(a) $50\ \Omega$ (b) $100\ \Omega$ (c) $200\ \Omega$ (d) $800\ \Omega$
2. In an ammeter 0.5% of main current passes through galvanometer. If resistance of galvanometer is G the resistance of ammeter will be
(a) $\frac{G}{200}$ (b) $\frac{G}{199}$ (c) $200G$ (d) $199G$
3. What type of galvanometer is used to prepare an ammeter or a voltmeter in the laboratory ?
(a) galvanometer (b) moving oil galvanometer
(c) neither @ nor (b) (d) ballastic galvanometer
4. In case of a moving coil galvanometer, what is the relation between the current I and the angle of deflection θ ?
(a) $I \propto \theta$ (b) $I \propto \frac{1}{\theta^2}$ (c) $I \propto \theta^2$ (d) $I \propto \frac{1}{\theta}$
5. How is a galvanometer converted into an ammeter ?
(a) by connecting a rightly chosen low resistance shunt in parallel to it.
(b) by connecting a high resistance shunt in parallel to it.
(c) by connecting low resistance in series with the galvanometer.
(d) by connecting high resistance in series with the galvanometer.
6. How should a resistance be connected with a galvanometer to convert it into a voltmeter ?
(a) in series (b) in parallel (c) neither in series nor in parallel
(d) both in series and parallel
7. What is the nature of magnetic field in a moving coil galvanometer ?
(a) varying (b) radial (c) circular (d) straight
8. A galvanometer is an electromagnetic device which is used to detect the presence of
(a) voltage in a circuit (b) e. m. f in a circuit (c) current in a circuit
(d) none of the above

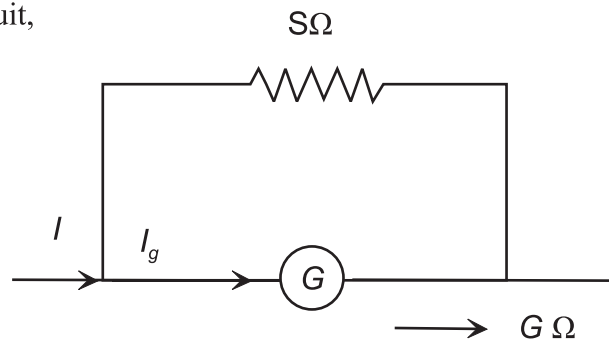9. When a voltmeter is connected in a circuit, the effective resistance of the circuit does not change due to
- (a) high resistance of voltmeter (b) low resistance of voltmeter
- (c) voltmeter connected in series (d) voltmeter connected in parallel
10. In a moving coil galvanometer of coil of N - turns of area A have a spring of stiffness k .
If coil is deflected by some angle Φ due to flow of I current in uniform radial magnetic field B , then
- (a) $\Phi = \left[\frac{NAB}{k} \right] I$ (b) $\Phi = \left[\frac{k}{BNA} \right] I$
- (c) $\Phi = \left[\frac{kA}{BN} \right] I$ (d) $\Phi = \left[\frac{BN}{kA} \right] I$
11. To make the field radial in a moving coil galvanometer
- (a) number of turns of coil is kept small (b) magnet is taken in the form of horse-shoe
- (c) poles are of very strong magnets (d) poles are cylindrically cut
12. In a moving coil galvanometer having a coil of N - turns of area A and carrying current I is placed in a radial field of strength B .
The torque acting on the coil is
- (a) $NA^2 B^2 I$ (b) $NAB I^2$ (c) $N^2 ABI$ (d) $NABI$
13. Current sensitivity of a galvanometer is
- (a) $\frac{NBA}{k}$ (b) $\frac{k}{NBA}$ (c) $\frac{NBA}{kR}$ (d) $\frac{kR}{NBA}$
14. For the given ammeter circuit,



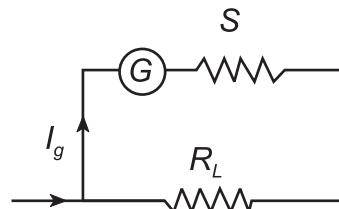- (a) $I_g S = IG$ (b) $(I - I_g)S = I_g G$ (c) $I_g G = (I + I_g)S$ (d) $\frac{I}{I_g} = \frac{G}{S}$
15. For the voltmeter circuit given,



- (a) $\frac{I_g}{I} = \frac{G}{S}$ (b) $\frac{I}{I_g} = \frac{R_L + G}{S}$
- (c) $(I - I_g)R_L = I_g (G + S)$ (d) $IR_L = I_g G$