

## ANSWER KEY – 3

### TOPIC – LOGIC GATES & COMBINATIONAL CIRCUITS

**SUBJECT: COMPUTER APPLICATION**

**F.M.: 15**


**CLASS: XII**

**DATE: 05.05.2020**

➤ Choose the correct option:

(1X15=15)

1) The following symbol is of:

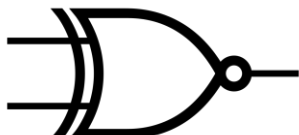

- (a) NOT                      (b) XOR                      (c) NAND                      **(d) XNOR**


2)  $\overline{A}B + A\overline{B}$  may also be represented as:

- (a)  $A \oplus B$**                       (b)  $\overline{A \oplus B}$                       (c)  $A \cdot B$                       (d)  $A + B$

3) How many NAND gate(s) are required to form a XOR gate? :

- (a) 1                      (b) 2                      (c) 4                      **(d) 5**

4) The following symbol is of:

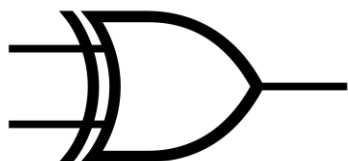

- (a) NOT                      **(b) XOR**                      (c) NAND                      (d) XNOR

5) How many NAND gate(s) are required to form a XNOR gate? :

- (a) 3                      **(b) 6**                      (c) 9                      (d) 12

6)  $\overline{A} \overline{B} + AB$  may also be represented as:

- (a)  $A \oplus B$                       **(b)  $\overline{A \oplus B}$**                       (c)  $A \cdot B$                       (d)  $A + B$

7) How many NOR gate(s) are required to form a XNOR gate? :

- (a) 5                      (b) 6                      **(c) 7**                      (d) 8

8) The minimum number of inputs required for XOR is:

- (a) 3                      **(b) 2**                      (c) 1                      (d) None of these

9) The minimum number of inputs required for XNOR is:

- (a) 4                      (b) 3                      **(c) 2**                      (d) 1

10)  $A \oplus B$  may also be represented as::

- (a)  $\overline{A}B + A\overline{B}$**                       (b)  $A \cdot B$                       (c)  $A + B$                       (d)  $\overline{A} \overline{B} + AB$

11) NAND gate is called an:

- (a) Uniform Gate                      **(b) Universal Gate**                      (c) Unilateral Gate                      (d) Unidigital Gate

12)  $\overline{A \oplus B}$  may also be represented as:

- (a)  $\overline{A}B + A\overline{B}$                       (b)  $A \cdot B$                       (c)  $A + B$                       **(d)  $\overline{A} \overline{B} + AB$**

13) How many complements on an expression don't change its value?:

- (a) 1                      **(b) 2**                      (c) 3                      (d) None of these

14) How many NOR gate(s) are required to form a XOR gate? :

- (a) 3                      **(b) 6**                      (c) 9                      (d) 12

15) All types of logic gates can be formed by suitable combinations of \_\_\_\_\_ gates only:

- (a) NOT                      (b) AND                      **(c) NOR**                      (d) XOR

\*\*\*

**PRITHWISH DE**