



# ST. LAWRENCE HIGH SCHOOL

A Jesuit Christian Minority Institution



## WORKSHEET – 40 (ANSWER KEY)

### Topic: Introduction and adder circuits

Subject: COMPUTER SCIENCE

Class - 11

F.M:15

Chapter: Combinational logic Circuit


Date: 27/02/2021

### Choose the correct answer for each question:

[5 X 1 = 15]


- The basic components of combinational circuits are/is:
  - Input variables
  - Logic gates
  - Output variables
  - All of these**
- How many half adders are required to construct a full adder?
  - 0
  - 1
  - 2**
  - 3
- At any instant of time, the output of the \_\_\_\_\_ depends only on the present input terminals.
  - Combinatory circuit
  - combinational circuit**
  - combiform circuit
  - combidigital circuit
- The difference between half adder and full adder is \_\_\_\_\_.
  - Half adder has two inputs while full adder has four inputs
  - Half adder has one output while full adder has two outputs
  - Half adder has two inputs while full adder has three inputs**
  - All of the Mentioned
- 3 bits full adder contains \_\_\_\_\_.
  - 3 combinational inputs
  - 4 combinational inputs
  - 6 combinational inputs
  - 8 combinational inputs**
- If A, B and C are the inputs of a full adder then the carry is given by \_\_\_\_\_.
  - A AND B OR (A OR B) AND C**
  - A OR B OR (A AND B) C
  - (A AND B) OR (A AND B)C
  - A XOR B XOR (A XOR B) AND C
- How many AND, OR and EXOR gates are required for the configuration of full adder?
  - 1, 2, 2

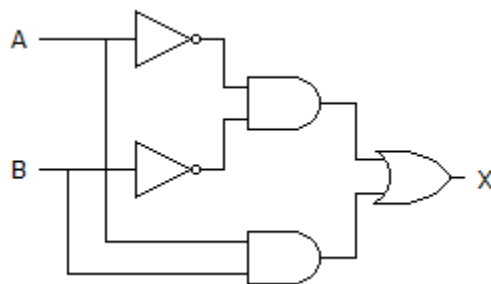- b) **2, 1, 2**  
 c) 3, 1, 2  
 d) 4, 0, 1
8. If A and B are the inputs of a half adder, the carry is given by \_\_\_\_\_  
 a) **A AND B**  
 b) A OR B  
 c) A XOR B  
 d) A EX-NOR B
9. Half-adders have a major limitation in that they cannot \_\_\_\_\_  
 a) Accept a carry bit from a present stage  
 b) Accept a carry bit from a next stage  
 c) **Accept a carry bit from a previous stage**  
 d) Accept a carry bit from the following stages
10. If A and B are the inputs of a half adder, the sum is given by \_\_\_\_\_  
 a) A AND B  
 b) A OR B  
 c) **A XOR B**  
 d) A EX-NOR B
11. In which operation carry is obtained?  
 a) Subtraction  
 b) **Addition**  
 c) Multiplication  
 d) Both addition and subtraction
12. If A, B and C are the inputs of a full adder then the sum is given by \_\_\_\_\_  
 a) A AND B AND C  
 b) A OR B AND C  
 c) **A XOR B XOR C**  
 d) A OR B OR C
13. Which of the following logic expressions represents the logic diagram shown?



- a)  $X = AB' + A'B$   
 b)  $X = (AB)' + AB$   
 c)  $X = (AB)' + A'B'$   
 d)  **$X = A'B' + AB$**

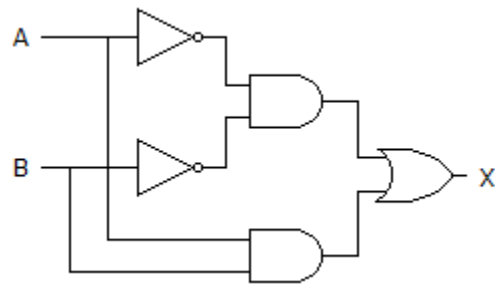14. What type of logic circuit is represented by the figure shown below?



- a) XOR
- b) **XNOR**
- c) AND
- d) XAND

15. Total number of inputs in a half adder is \_\_\_\_\_

- a) **2**
- b) 3
- c) 4
- d) 1

Phalguni Pramanik