



# ST. LAWRENCE HIGH SCHOOL

A Jesuit Christian Minority Institution



## WORKSHEET -15(ANSWER KEY)

### Topic – Introduction to Sequential Logic Circuits

Subject: COMPUTER SCIENCE

Class - 12

F.M:15

Chapter: Sequential Logic Circuits


Date: 18/06/2020

### Choose the correct answer for each question:

**15x1=15**


1. What is/are the crucial function/s of memory elements used in the sequential circuits?
  - a. Storage of binary information
  - b. Specify the state of sequential
  - c. **Both a & b**
  - d. None of the above
2. How are the sequential circuits specified in terms of time sequence?
  - a. By Inputs
  - b. By Outputs
  - c. By Internal States
  - d. **All of the above**
3. The behaviour of synchronous sequential circuit can be predicted by defining the signals at \_\_\_\_\_.
  - a. **discrete instants of time**
  - b. continuous instants of time
  - c. sampling instants of time
  - d. at any instant of time

 4. The output of a sequential circuit depends on
- a. Present inputs only
  - b. Past outputs only
  - c. **Both present and past inputs**
  - d. Present outputs only
5. The clock signals are used in sequential logic circuits to
- a. Tell the time of the day
  - b. Tell how much time has elapsed since the system was turned on
  - c. Carry parallel data signals
  - d. **Synchronize events in various parts of system**
6. Synchronous Sequential circuits can be used in :
- a. Synchronous counters
  - b. Flip-flops
  - c. **Both (a) and (b)**
  - d. None of these
7. The following diagram represents :



- a. **Positive edge triggering**
- b. Negative edge triggering
- c. Level triggering
- d. None of these

8. The following diagram represents:

 

- a. Positive edge triggering
- b. Negative edge triggering**
- c. Level triggering
- d. None of these

9. \_\_\_\_\_ allows a circuit to become active at the positive or negative edge of the clock signal.

- a. Positive level triggering
- b. Negative level triggering
- c. Edge triggering**
- d. None of these

10. In \_\_\_\_\_, an event occurs during the high voltage or low voltage.

- a. Positive edge triggering
- b. Negative edge triggering
- c. Level triggering**
- d. None of these

11. Flip-flops are:

- a. Level-triggered
- b. Edge-triggered**
- c. Both (a) and (b)

d. None of these

12. Latches are:


a. Level-triggered

b. Edge-triggered

c. Both (a) and (b)

d. None of these

13. The following diagram represents:

 

a. Positive level triggering

b. Negative level triggering

c. Edge triggering

d. None of these

14. \_\_\_\_\_ acts as a memory element for one bit of data.

a. Flip-flop


b. Clock pulse

c. Input pulse

d. Output signal

15. The following diagram represents:

Triggering on low clock level

 

- a. Positive level triggering
- b. Negative level triggering**
- c. Edge triggering
- d. None of these

Phalguni Pramanik