

ST. LAWRENCE HIGH SCHOOL



A Jesuit Christian Minority Institution

WORKSHEET - 22

Topic – Logic Gates

Chapter: Boolean Algebra	Date: 15/08/2020
Chaosa the correct answer for each question.	[[V 4 - 45]
<u>Choose the correct answer for each question.</u>	$[5 \mathbf{X} \mathbf{I} = 15]$
a) AND	
b) OB	
c) EXOR	
d) NOR	
2. Which of the following gate will give a 0 when both of its in	nputs are 1?
a) AND	
b) OR	
c) NAND	
d) EXOR	
3. The gate which is used to reverse the output obtained is _	
a) NOR	
b) NAND	
c) EXOR	
d) NUI	
4. The output of an AND gate with three inputs, A, B, and C, E	s high when
b) $A = 0$ $B = 1$ $C = 0$	
c) $A = 1, B = 1, C = 1$	
d) $A = 1, B = 0, C = 0$	
5. Which of following are known as universal gates?	
a) NAND & NOR	
b) AND & OR	
c) XOR & OR	
d) EX-NOR & XOR	
6. If a 3-input NOR gate has eight input possibilities, how man	ny of those possibilities
will result in a HIGH output?	
a) 1	
b) 6	
c) 7	
d) 8	

7. The logic gate that will have HIGH or "1" at its output when any one of its inputs is HIGH is a/an gate.

a) AND

- b) OR
- c) EXOR
- d) NOR
- 8. The output of a logic gate is 1 when all the input are at logic 0 as shown below:

INF	TUT	OUTPUT
А	В	С
0	0	1
0	1	0
1	0	0
1	1	0

INP	UT	OUTPUT
А	В	С
0	0	1
0	1	0
1	0	0
1	1	1

The gate is either _____ a) A NAND or an EX-OR

b) An OR or an EX-NORc) An AND or an EX-ORd) A NOR or an EX-NOR

- How many two input AND gates and two input OR gates are required to realize Y = BD + CE + AB?
 - a) 3, 2
 - b) 4, 2
 - c) 1, 1
 - d) 2, 3

10. The NOR gate output will be high if the two inputs are _____

- a) 00
- b) 01
- c) 10
- d) 11
- 11. How many AND gates are required to realize Y = CD + EF + G?
 - a) 4
 - b) 5
 - c) 3
 - d) 2
- 12. Both OR and AND gates can have only two inputs:
 - a. True
 - b. False

13. The output will be a LOW for any case when one or more inputs are zero in a/an

a) AND

- b) OR
- c) EXOR
- d) NOR

14. How many two-input AND and OR gates are required to realize Y = CD+EF+G?

- a) 2*,* 2
- b) 2, 3
- c) 3, 3
- d) 3*,* 2

15. The boolean expression of an OR gate is _____

- a) A.B
- b) A'B+AB'
- c) A+B
- d) A'B'

Phalguni Pramanik