



ANSWER KEY – 1

TOPIC – LOGIC GATES & COMBINATIONAL CIRCUITS

SUBJECT: COMA

F.M.: 15

CLASS: XII

DATE: 02.05.2020

➤ Choose the correct option:

(1X15=15)

1) Which of the following is a basic logic gate? :

- (a) **NOT** (b) NOR (c) NAND (d) XOR

2) Which of the following is an Universal gate? :

- (a) NOT (b) AND (c) **NAND** (d) XOR

3) Which of the following is an Exclusive gate? :

- (a) NOT (b) AND (c) NAND (d) **XOR**

4) Which of the following is true for NAND gate? :

- (a) **1 NAND 1 = 0** (b) 1 NAND 1=1 (c) 0 NAND 0=0 (d) both (b) & (c)

5) Which of the following is true for AND gate? :

- (a) 1.1 = 0 (b) 1.1=1 (c) 0.0=0 (d) **both (b) & (c)**

6) Which gate may be termed as inverter? :

- (a) **NOT** (b) AND (c) NAND (d) XOR

7) What is the output for $\overline{1 + 0}$? :

- (a) 1 (b) **0** (c) 10 (d) None of these

8) What is the output for $\overline{1.0}$? :

- (a) **1** (b) 0 (c) 10 (d) None of these

9) What is the output for $\overline{1}$? :

- (a) 1 (b) **0** (c) 10 (d) None of these

10) Which gate is the logical complement of XOR? :

- (a) NOT (b) NOR (c) NAND (d) **XNOR**

11) Which gate is the logical complement of OR? :

- (a) NOT (b) **NOR** (c) NAND (d) XNOR

12) Which gate works with one input? :

- (a) **NOT** (b) NOR (c) NAND (d) XNOR

13) How many states are possible with 2 inputs? :

- (a) 1 (b) 2 (c) 3 **(d) 4**

14) A logic gate has how many outputs? :

- (a) 0 **(b) 1** (c) 2 (d) 3

15) The complement of the AND gate is called:

- (a) NOT (b) NOR **(c) NAND** (d) XNOR
