



ST. LAWRENCE HIGH SCHOOL

A Jesuit Christian Minority Institution



WORKSHEET -17 (ANSWER KEY)

Topic – SR Flip-flop

Subject: COMPUTER SCIENCE

Class - 12

F.M:15

Chapter: Sequential Logic Circuits

Date: 20/06/2020

Choose the correct answer for each question:

[15 X 1 = 15]

- The logic circuits whose outputs at any instant of time depends only on the present input but also on the past outputs are called:
 - Combinational circuits
 - Sequential circuits**
 - Latches
 - Flip-flops
- A basic S-R flip-flop can be constructed by cross-coupling of which basic logic gates?
 - AND or OR gates
 - XOR or XNOR gates
 - NOR or NAND gates**
 - AND or NOR gates
- How many VALID entries of the truth table for an S-R flip-flop have?
 - 1
 - 2
 - 3**
 - 4
- Latch together with a triggering circuit form a:
 - inductor
 - flip-flop**
 - timing generator
 - sine generator
- One example of the use of an S-R flip-flop is as _____
 - Transition pulse generator
 - Racer
 - Switch debouncer**
 - Astable oscillator
- How many NAND gates are required to construct SR flip flop?
 - four
 - three
 - two**
 - one

7. A basic S-R flip-flop can be constructed by cross-coupling of which basic logic gates?
- a) AND or OR gates
 - b) XOR or XNOR gates
 - c) **NOR or NAND gates**
 - d) AND or NOR gates
8. In S-R flip-flop, if $Q = 0$ the output is said to be _____
- a) Set
 - b) **Reset**
 - c) Previous state
 - d) Current state
9. When set input of a S-R flip-flop is high and $R=0$, the output will _____
- a) Be invalid
 - b) Change
 - c) Not change
 - d) **high**
10. Which state is undefined in SR flip-flop?
- a) $S=0, R=0$
 - b) $S=0, R=1$
 - c) $S=1, R=0$
 - d) **$S=1, R=1$**
11. Race condition occurs in:
- a) Synchronous
 - b) **Asynchronous**
 - c) Combinational
 - d) All of the above
12. The full form of SR in SR flip-flop is _____
- a) System rated
 - b) **Set reset**
 - c) Set ready
 - d) Set Rated
13. It is present in flip-flop, but absent in latch:
- a) input state
 - b) output state
 - c) inverter
 - d) **clock**
14. What is the output of SR flip-flop for the following input: $S=0$ and $R=0$?
- a) set
 - b) **reset**
 - c) undefined
 - d) unchanged

15. One major difference between a NAND based S' - R' latch & a NOR based S-R latch is :
- a) **The inputs of NOR latch are 0 but 1 for NAND latch**
 - b) The inputs of NOR latch are 1 but 0 for NAND latch
 - c) The output of NAND latch becomes set if $S'=0$ & $R'=1$ and vice versa for NOR latch
 - d) The output of NOR latch is 1 but 0 for NAND latch

Phalguni Pramanik