



WORKSHEET – 10
TOPIC – LOGIC GATES & COMBINATIONAL CIRCUITS

SUBJECT: COMPUTER APPLICATION
F.M.: 15

CLASS: XII
DATE: 13.05.2020

➤ **Choose the correct option:**

(1X15=15)

- 1) An octal to binary encoder circuit has how many input lines?:
(a) 4 (b) 6 (c) 8 (d) 10

- 2) A decimal to binary encoder circuit has how many input lines?:
(a) 4 (b) 6 (c) 8 (d) 10

- 3) An octal to binary encoder circuit has how many output lines?:
(a) 3 (b) 6 (c) 8 (d) 10

- 4) A decimal to binary encoder circuit has how many input lines?:
(a) 4 (b) 6 (c) 8 (d) 10

- 5) Encoder is functionally opposite to:
(a) Multiplexer (b) De-multiplexer (c) Decoder (d) None of these

- 6) Encoder is a/an _____ circuit:
(a) Even (b) Combinational (c) Sequential (d) None of these

- 7) The number of OR gates required for octal to binary encoder is:
(a) 4 (b) 0 (c) 8 (d) 3

- 8) The number of AND gates required for octal to binary encoder is:
(a) 4 (b) 0 (c) 8 (d) 3

- 9) The number of OR gates required for decimal to binary encoder is:
(a) 4 (b) 0 (c) 8 (d) 3

- 10) The number of AND gates required for decimal to binary encoder is:
(a) 4 (b) 0 (c) 8 (d) 3

11) If we record any music in any recorder, such types of process are called _____:

- (a) Multiplexing (b) Decoding (c) Demultiplexing (d) Encoding

12) How is an encoder different from a decoder?:

- (a) The output of an encoder is a binary code for 1-of-N input
(b) The output of a decoder is a binary code for 1-of-N input
(c) The output of an encoder is a binary code for N-of-1 output
(d) The output of a decoder is a binary code for N-of-1 output

13) Which of the following are building blocks of encoders?:

- (a) NOT gate (b) OR gate (c) AND gate (d) NAND gate

14) Device which converts an input device state into a binary representation of ones or zeros is termed as:

- (a) Multiplexer (b) De-multiplexer (c) Decoder (d) Encoder

15) How many OR gates are requires for a Decimal-to-BCD encoder?:

- (a) 2 (b) 4 (c) 6 (d) 8

PRITHWISH DE