



WORKSHEET – 1

TOPIC – LOGIC GATES & COMBINATIONAL CIRCUITS

SUBJECT: COMA
F.M.: 15

CLASS: XII
DATE: 02.05.2020

➤ Choose the correct option:

(1X15=15)

1) Which of the following is a basic logic gate? :

- (a) NOT (b) NOR (c) NAND (d) XOR

2) Which of the following is an Universal gate? :

- (a) NOT (b) AND (c) NAND (d) XOR

3) Which of the following is an Exclusive gate? :

- (a) NOT (b) AND (c) NAND (d) XOR

4) Which of the following is true for NAND gate? :

- (a) $1 \text{ NAND } 1 = 0$ (b) $1 \text{ NAND } 1 = 1$ (c) $0 \text{ NAND } 0 = 0$ (d) both (b) & (c)

5) Which of the following is true for AND gate? :

- (a) $1.1 = 0$ (b) $1.1 = 1$ (c) $0.0 = 0$ (d) both (b) & (c)

6) Which gate may be termed as inverter? :

- (a) NOT (b) AND (c) NAND (d) XOR

7) What is the output for $\overline{1 + 0}$? :

- (a) 1 (b) 0 (c) 10 (d) None of these

8) What is the output for $\overline{1.0}$? :

- (a) 1 (b) 0 (c) 10 (d) None of these

9) What is the output for $\overline{1}$? :

- (a) 1 (b) 0 (c) 10 (d) None of these

10) Which gate is the logical complement of XOR? :

- (a) NOT (b) NOR (c) NAND (d) XNOR

11) Which gate is the logical complement of OR? :

- (a) NOT (b) NOR (c) NAND (d) XNOR

12) Which gate works with one input? :

- (a) NOT (b) NOR (c) NAND (d) XNOR

13) How many states are possible with 2 inputs? :

- (a) 1 (b) 2 (c) 3 (d) 4

14) A logic gate has how many outputs? :

- (a) 0 (b) 1 (c) 2 (d) 3

15) The complement of the AND gate is called:

- (a) NOT (b) NOR (c) NAND (d) XNOR
