



# ST. LAWRENCE HIGH SCHOOL

A Jesuit Christian Minority Institution



## WORKSHEET - 22 (ANSWER KEY)

### Topic – Logic Gates

Subject: COMPUTER SCIENCE

Class - 11

F.M:15

Chapter: Boolean Algebra

Date: 15/08/2020

### Choose the correct answer for each question:

[5 X 1 = 15]

1. A \_\_\_\_\_ gate gives the output as 1 only if all the inputs signals are 1.  
a) **AND**  
b) OR  
c) EXOR  
d) NOR
2. Which of the following gate will give a 0 when both of its inputs are 1?  
a) AND  
b) OR  
c) **NAND**  
d) EXOR
3. The gate which is used to reverse the output obtained is \_\_\_\_\_.  
a) NOR  
b) NAND  
c) EXOR  
d) **NOT**
4. The output of an AND gate with three inputs, A, B, and C, is HIGH when \_\_\_\_\_.  
a) A = 1, B = 1, C = 0  
b) A = 0, B = 1, C = 0  
c) **A = 1, B = 1, C = 1**  
d) A = 1, B = 0, C = 0
5. Which of following are known as universal gates?  
a) **NAND & NOR**  
b) AND & OR  
c) XOR & OR  
d) EX-NOR & XOR
6. If a 3-input NOR gate has eight input possibilities, how many of those possibilities will result in a HIGH output?  
a) **1**  
b) 6  
c) 7  
d) 8

7. The logic gate that will have HIGH or "1" at its output when any one of its inputs is HIGH is a/an ..... gate.

a) AND

b) **OR**

c) EXOR

d) NOR

8. The output of a logic gate is 1 when all the input are at logic 0 as shown below:

INPUT		OUTPUT
A	B	C
0	0	1
0	1	0
1	0	0
1	1	0

INPUT		OUTPUT
A	B	C
0	0	1
0	1	0
1	0	0
1	1	1

The gate is either \_\_\_\_\_

a) A NAND or an EX-OR

b) An OR or an EX-NOR

c) An AND or an EX-OR

d) **A NOR or an EX-NOR**

9. How many two input AND gates and two input OR gates are required to realize  $Y = BD + CE + AB$ ?

a) **3, 2**

b) 4, 2

c) 1, 1

d) 2, 3

10. The NOR gate output will be high if the two inputs are \_\_\_\_\_

a) **00**

b) 01

c) 10

d) 11

11. How many AND gates are required to realize  $Y = CD + EF + G$ ?

a) 4

b) 5

c) 3

d) **2**

12. Both OR and AND gates can have only two inputs:

a. True

b. **False**

13. The output will be a LOW for any case when one or more inputs are zero in a/an
- a) **AND**
  - b) OR
  - c) EXOR
  - d) NOR
14. How many two-input AND and OR gates are required to realize  $Y = CD + EF + G$ ?
- a) **2, 2**
  - b) 2, 3
  - c) 3, 3
  - d) 3, 2
15. The boolean expression of an OR gate is \_\_\_\_\_
- a)  $A.B$
  - b)  $A'B + AB'$
  - c)  **$A+B$**
  - d)  $A'B'$

Phalguni Pramanik