



8. From Q. 7, find the main current flowing through R is

- (a) $I = \frac{mne}{mR+nr}$ (b) $I = \frac{mne}{mr+nR}$ (c) $I = \frac{mnrR}{e}$ (d) $\frac{mR+nr}{mne}$

Ans. : (a) $I = \frac{mne}{mR+nr}$

9. Two electric cells each of emf $1.5V$ and internal resistance 2Ω are connected in parallel and this combination of cells is connected with an external resistance of 2Ω . What will be the current in the external circuit?

- (a) $\frac{1}{4}A$ (b) $\frac{1}{3}A$ (c) $\frac{1}{2}A$ (d) $1A$

Ans. : (c) $\frac{1}{2}A$

10. n identical cells, each of emf e and internal resistance r , are first connected in series and then in parallel. What will be the ratio of the emfs and of the internal resistances of these two cell combinations?

- (a) n, n (b) n, n^2 (c) n^2, n (d) $\frac{1}{n}, n$

Ans. : (b) n, n^2

11. A galvanometer connected with an unknown resistor and two identical cells in series each of emf $2V$, shows a current of $1A$. If the cells are connected in parallel, it shows $0.8A$. Then the internal resistance of the cell is

- (a) 1Ω (b) 2.8Ω (c) 0.7Ω (d) 1.4Ω

Ans. : (a) 1Ω

12. The n rows each containing m cells in series are joined in parallel. Maximum current is taken from this combination across an external resistance of 3Ω resistance. If the total number of cells used are 24 and internal resistance of each cell is 0.5Ω then

- (a) $m = 8, n = 3$ (b) $m = 6, n = 4$ (c) $m = 12, n = 2$ (d) $m = 2, n = 12$

Ans. : (c) $m = 12, n = 2$


13. In a mixed grouping of identical cells 5 rows are connected in parallel by each row containing 10 cells. This combination sends a current i through an external resistance of 20Ω . If the emf and internal resistance of each cell is 1.5 volt and 1Ω respectively then the value of i is

- (a) 0.14 (b) 0.25 (c) 0.75 (d) 0.68 Ans. : (d) 0.68

14. A group of N cells whose emf varies directly with the internal resistance as per the equation $E_N = 1.5r_N$ are connected as shown in the following figure. The current i in the circuit is

- (a) 0.51 amp
(b) 5.1 amp
(c) 0.15 amp
(d) 1.5 amp

Ans. : (d) 1.5 amp

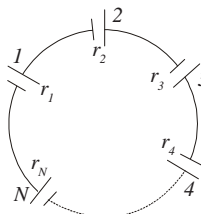

15. 100 cells each of emf $5V$ and internal resistance 1Ω are to be arranged so as to produce maximum current in a 25Ω resistance. Each row contains equal number of cells. The number of rows should be

- (a) 2 (b) 4 (c) 5 (d) 100 Ans. : (a) 2