



ST. LAWRENCE HIGH SCHOOL

A Jesuit Christian Minority Institution



WORKSHEET -21

Topic – Serial and Parallel Registers

Subject: COMPUTER SCIENCE

Class - 12

F.M:15

Chapter: Sequential Logic Circuits

Date: 25/06/2020

Choose the correct answer for each question:

[15 X 1 = 15]

1. A register is defined as :
 - a. The group of latches for storing one bit of information
 - b. The group of latches for storing n-bit of information
 - c. The group of flip-flops suitable for storing one bit of information
 - d. The group of flip-flops suitable for storing binary information
2. A register can also be used to provide data movements.
 - a. Shift register
 - b. Serial register
 - c. Simple register
 - d. All of these
3. The register is a type of :
 - a. Sequential circuit
 - b. Combinational circuit
 - c. CPU
 - d. Latches
4. There are _____ basic types of register.
 - a. Six
 - b. Four
 - c. One
 - d. Many
5. Shift registers having four bits will enable the shift control for:
 - a. 2 clock pulses
 - b. 3 clock pulses
 - c. 4 clock pulses
 - d. 5 clock pulses
6. Time to transfer the content of shift register is called:
 - a. Word duration
 - b. Clock duration
 - c. Duration
 - d. Bit time
7. Register performing shift in one direction is called:
 - a. Unidirectional shift register
 - b. Bidirectional shift register
 - c. Left shift register
 - d. Right shift register

8. One bit transfer of the information at a time is called:
 - a. Serial transfer
 - b. Parallel transfer
 - c. Shifting
 - d. Rotating
9. The type of register in which data is entered into it only one bit at a time, but has all data bits available as output is:
 - a. SISO
 - b. PISO
 - c. SIPO
 - d. PIPO
10. The type of register in which we have access to left most and right most flip flop is:
 - a. SISO
 - b. PISO
 - c. SIPO
 - d. PIPO
11. This type of register accepts inputs and outputs data serially:
 - a. PIPO
 - b. PISO
 - c. SIPO
 - d. SISO
12. How can parallel data be taken out of a shift register simultaneously?
 - a. Use the Q output of the first FF
 - b. Use the Q output of the last FF
 - c. Tie all of the Q outputs together
 - d. Use the Q output of each FF
13. What is meant by parallel load of a shift register?
 - a. All FFs are preset with data
 - b. Each FF is loaded with data, one at a time
 - c. Parallel shifting of data
 - d. All FFs are set with data
14. How many methods of shifting of data are available?
 - a. 2
 - b. 3
 - c. 4
 - d. 5
15. In parallel shifting method, data shifting occurs _____
 - a. One bit at a time
 - b. Simultaneously
 - c. Two bit at a time
 - d. Four bit at a time