



ST. LAWRENCE HIGH SCHOOL

A Jesuit Christian Minority Institution



WORKSHEET -21(ANSWER KEY)

Topic – Serial and Parallel Registers

Subject: COMPUTER SCIENCE

Class - 12

F.M:15

Chapter: Sequential Logic Circuits

Date: 25/06/2020

Choose the correct answer for each question:

[15 X 1 = 15]

1. A register is defined as :
 - a. The group of latches for storing one bit of information
 - b. The group of latches for storing n-bit of information
 - c. The group of flip-flops suitable for storing one bit of information
 - d. **The group of flip-flops suitable for storing binary information**
2. A register can also be used to provide data movements.
 - a. **Shift register**
 - b. Serial register
 - c. Simple register
 - d. All of these
3. The register is a type of :
 - a. **Sequential circuit**
 - b. Combinational circuit
 - c. CPU
 - d. Latches
4. There are _____ basic types of register.
 - a. Six
 - b. **Four**
 - c. One
 - d. Many
5. Shift registers having four bits will enable the shift control for:
 - a. 2 clock pulses
 - b. 3 clock pulses
 - c. **4 clock pulses**
 - d. 5 clock pulses
6. Time to transfer the content of shift register is called:
 - a. **Word duration**
 - b. Clock duration
 - c. Duration
 - d. Bit time
7. Register performing shift in one direction is called:
 - a. **Unidirectional shift register**
 - b. Bidirectional shift register
 - c. Left shift register
 - d. Right shift register

8. One bit transfer of the information at a time is called:
- Serial transfer**
 - Parallel transfer
 - Shifting
 - Rotating
9. The type of register in which data is entered into it only one bit at a time, but has all data bits available as output is:
- SISO
 - PISO
 - SIPO**
 - PIPO
10. The type of register in which we have access to left most and right most flip flop is:
- SISO**
 - PISO
 - SIPO
 - PIPO
11. This type of register accepts inputs and outputs data serially:
- PIPO
 - PISO
 - SIPO
 - SISO**
12. How can parallel data be taken out of a shift register simultaneously?
- Use the Q output of the first FF
 - Use the Q output of the last FF
 - Tie all of the Q outputs together
 - Use the Q output of each FF**
13. What is meant by parallel load of a shift register?
- All FFs are preset with data**
 - Each FF is loaded with data, one at a time
 - Parallel shifting of data
 - All FFs are set with data
14. How many methods of shifting of data are available?
- 2**
 - 3
 - 4
 - 5
15. In parallel shifting method, data shifting occurs _____
- One bit at a time
 - Simultaneously**
 - Two bit at a time
 - Four bit at a time